

### 23.5.3 Physics Paper 3 (232/3)

Name ..... Index Number .....

232/3

PHYSICS

PRACTICAL

Paper 3

Oct./ Nov. 2006

2½ hours

### THE KENYA NATIONAL EXAMINATIONS COUNCIL

Kenya Certificate of Secondary Education

PHYSICS

PRACTICAL

Paper 3

2½ hours

Write your name and index number in the spaces provided above.

Answer ALL the questions in the spaces provided in the question paper.

You are supposed to spend the first 15 minutes of the 2½ hours allowed for this paper reading the whole paper carefully before commencing your work.

Marks are given for a clear record of the observations actually made, their suitability, accuracy, and the use made of them.

Candidates are advised to record their observations as soon as they are made.

Mathematical tables and electronic calculators may be used.

#### For Examiner's Use Only

##### Question 1

	a	b(i)	b(ii)	c	d(i)	d(ii)	d(iii)
Maximum Score	2	1	1	6	5	3	2
Candidate's Score							

Total

##### Question 2

	a	b(i)	b(ii)	b(iii)	d	e(i)	e(ii)	f	g
Maximum Score	3	2	1	1	3	5	1	2	2
Candidate's Score									

Total

Grand Total

Candidates should check the question paper to ensure that all the pages are printed as indicated and no questions are missing.

### QUESTION ONE

You are provided with the following:

- a glass marble
- a stop watch
- a 105 cm plastic tube split open with a mark near one end
- vernier callipers (to be shared)
- a metre rule or half-metre rule
- a balance (to be shared)
- retort stand, one boss and one clamp.

Proceed as follows:

- (a) Use the vernier callipers provided to measure the diameter of the marble and hence determine the radius.

Diameter of the marble = .....cm

Radius of the marble  $r$  = .....cm

- (b) (i) Using the balance provided obtain the mass  $M$  of the marble.

$M$  = .....g

- (ii) Determine the constant  $P$  given that  $P = 0.4 Mr^2$ .

The experiment involves timing a marble as it runs down the split tube as a runway.

- (c) Clamp the marked end of the split tube with the inside uppermost. Ensure the end with the mark is on the greater slope. Raise this end such that the mark is at a height  $h = 8$  cm above the bench level. The other end should rest on the bench as shown in figure 1.

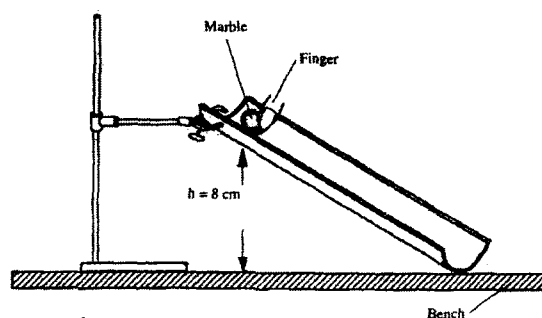


Figure 1

Place the marble at the mark on the runway and hold it in place gently with the finger as shown in the figure 1. By simultaneously releasing the ball and starting the stop watch measure and record in table 1, the time,  $t$ , taken by the marble to reach the lower end of the runway. (It is advisable to measure the time twice and record the average value).

Vary the height  $h$ , to other values shown in table 1. Measure and record in the table the corresponding average values of  $t$ . Complete the table.

Table 1

height, h (cm)	8	9	10	11	12	13	14	15
Average time, t (s)								
t <sup>2</sup> (s <sup>2</sup> )								
$\frac{1}{h}$ (cm <sup>-1</sup> )								

(d) (i) On the grid provided plot the graph of t<sup>2</sup> (y-axis) against  $\frac{1}{h}$ .

(ii) Determine the slope S of the graph.

(iii) Determine the constant G for the marble given that

$$G = Mr^2 \left( \frac{S}{20} - 1 \right)$$

## QUESTION TWO

You are provided with the following:

- a voltmeter
- two dry cells and a cell holder
- a switch
- a resistor labelled R (4Ω)
- a wire mounted on a mm scale and labelled G
- a micrometer screw gauge (to be shared)
- six connecting wires with six crocodile clips.

Proceed as follows:

(a) Record the length L<sub>0</sub> of the wire labelled G.

L<sub>0</sub> = .....

Use the micrometer screw gauge provided to measure the diameter of the wire labelled G at two different points and determine the average diameter, d.

The diameter d<sub>1</sub> = ..... mm, d<sub>2</sub> = .....mm

Average diameter d = ..... mm

Determine the radius r of the wire in metres.

Radius r = ..... m

- (b) Set up the apparatus as shown in the circuit diagram in figure 2.

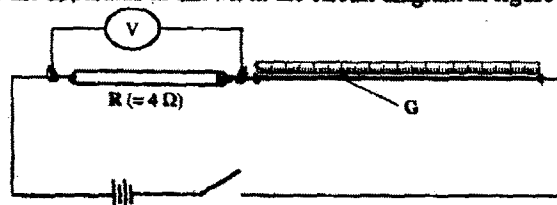


Figure 2

- (i) Use the voltmeter provided to measure the p.d,  $V_R$  across R and the p.d,  $V_G$  across G when the switch is closed.

$V_R = \dots\dots\dots$  Volts

$V_G = \dots\dots\dots$  Volts

Open the switch.

- (ii) Use the value of R provided and the value of  $V_R$  in b (i) above to calculate the current I flowing through R when the switch was closed.

$I = \dots\dots\dots$  Amperes

- (iii) Determine the constant H given that

$$H = \frac{100V_G}{I \times L_G}$$

$H = \dots\dots\dots \Omega m^{-1}$

- (c) Connect the voltmeter across R as shown in figure 3.

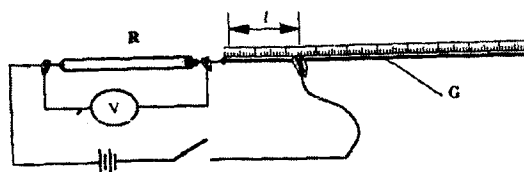


Figure 3

Adjust the position of one crocodile clip on the wire G to a point such that the length  $l$  of the wire in the circuit is 5 cm. (see figure 3). Close the switch.

Read and record in table 2, the value of the p.d. across R. Open the switch.

- (d) Repeat the procedure in (c) above for the other values of  $l$  shown in table 2.

Table 2

Distance $l$ (cm)	0	5	10	20	30	40	60	70
p.d. V across R(V)								

- (e) (i) On the grid provided plot the graph of V (y-axis) against  $l$ .

- (ii) From the graph, determine  $l_1$ , the value of  $l$  when  $V = \frac{V_0}{2}$  where  $V_0$  is the p.d. where  $l = 0$ .

- (f) Determine the constant  $D$  for the wire given that

$$D = \frac{R}{l_1} \times \frac{300}{v_0}$$

- (g) Determine the constant  $\rho$  given that

$$\rho = \frac{\pi r^2}{2} (D + H), \text{ where } r \text{ is the radius of the wire in metres.}$$